

G. Cai praneeth
(240102027)

* 2 stage OTA design Assignment:

Given $V_{Tn} = 0.37V$; $V_{Tp} = 0.39V$

$\mu_n C_{ox} = 230 \mu A/V^2$; $\mu_p C_{ox} = 100 \mu A/V^2$


$V_{dd} = 0.18 \times 10 V$; $L_{min} = 0.18 \mu m$; $W_{min} = 0.27 \mu m$.

* Choose tail current $= 50 \mu A$, $I_{ref} = 5 \mu A$.

Current through $M_1, M_2, M_3, M_4 = 25 \mu A$.

By assuming overdrive for M_1, M_2 is $100 mV = 0.1V$

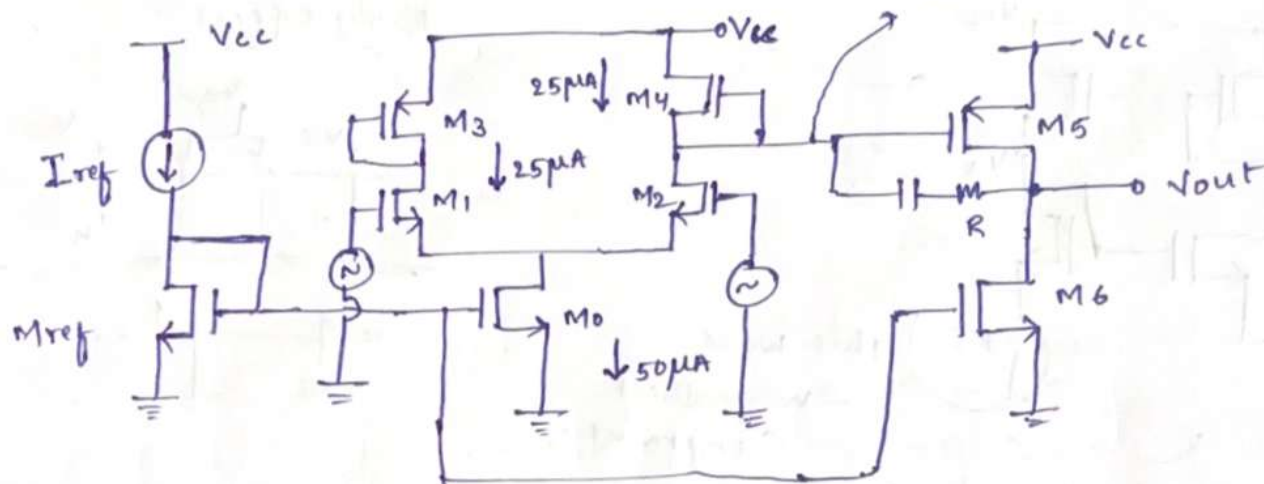assume DC Voltage $\approx 1V = \frac{V_{cc}}{2}$



$$I_D \approx \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_{th})^2$$

$$\mu_n C_{ox} = 230 \mu A/V^2$$

$$25 \mu A = \frac{1}{2} (230 \times 10^{-6}) \left(\frac{W}{L} \right) (0.1)^2$$

$$\frac{W}{L} \approx 21.74$$

* Choose

$$\begin{aligned} L_1 &= 1 \mu m \\ W_1 &= 21.74 \mu m \end{aligned}$$

* Since same current is flowing through M_2 :

$$L_2 = 1 \mu m, W_2 = 21.74 \mu m$$

* for better gain $M_{ref} \Rightarrow$

$$\begin{aligned} L &= 1 \mu m \\ W &= 10 \mu m \end{aligned}$$

* since

$$I_{tail} = 10 \times I_{ref}$$

$\Rightarrow$

$$\begin{aligned} L_0 &= 1 \mu m \\ W_0 &= 100 \mu m \end{aligned}$$

for $M_3 \Rightarrow I_D = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right) (V_{gs} - V_{th})^2$
 $2 \times 25 \times 10^{-6} = 100 \times 10^{-6} \times \frac{W}{L} \times (V_{gs} - V_{th})^2$

for pmos, $V_{sg} - V_{th} = V_{cc} - V_G - (V_{tp})_{pmos}$
 $= 1.8V - 1V - 0.39V$
 $= 0.41V$

$50 \times 10^{-6} = 100 \times 10^{-6} \times \frac{W}{L} \times (0.41)^2$

$\frac{W}{L} \approx 2.974$

* Choose $\begin{cases} L_3 = 1\mu m \\ W_3 = 2.974\mu m \end{cases}$

* Since same current passing through M_4

$\begin{cases} L_4 = 1\mu m, W_4 = 2.974\mu m \end{cases}$

* As we know the current passing through $I_6 = 50\mu A = I_5$

So $\left(\frac{W}{L} \right)_5 = 2 \left(\frac{W}{L} \right)_3$

$\begin{cases} L_5 = 1\mu m, W_5 = 5.948\mu m \end{cases}$

$\begin{cases} L_6 = 1\mu m, W_6 = 100\mu m \end{cases}$

By taking $V_{gs} - V_{th} = 0.1V$

theoretical $g_{m1} = \frac{2I_1}{V_{gs} - V_{th}} = \frac{2 \times 25 \times 10^{-6}}{0.1}$

$\begin{cases} g_{m1} = 5 \times 10^{-4} \end{cases}$

simulated $g_{m1} \approx 4.2 \times 10^{-4}$

$r_{o4} = \frac{1}{G_{ds4}} = \frac{1}{1.00 \times 10^{-6}} = 10^6$

$r_{o2} = \frac{1}{G_{ds2}} = \frac{1}{2.99 \times 10^{-6}} = 3.3 \times 10^5$

By simulation we got the values

$r_{o1} || r_{o2} = 2.48 \times 10^5$

$$\begin{aligned} * \text{ gain of stage 1} &= g_{m1} (r_{o1} || r_{o2}) \\ &\approx 4.2 \times 10^{-4} (2.48 \times 10^5) \\ &= 104.16 \end{aligned}$$

$$20 \log(\text{gain}) = 20 \log(104.16) \approx 40 \text{ dB}$$

* gain of stage 2

$$g_{m5} = \frac{2I_5}{V_{sg} - V_{th}} = \frac{2 \times 50 \times 10^{-6}}{0.582} = 1.71 \times 10^{-4}$$

$$\text{simulated } g_{m5} = 1.63 \times 10^{-4}$$

$$\left. \begin{aligned} r_{o5} &= \frac{1}{G_{ds5}} = \frac{1}{2.39 \times 10^{-6}} = 4.18 \times 10^5 \\ r_{o6} &= \frac{1}{G_{ds6}} = \frac{1}{6.47 \times 10^{-6}} = 1.54 \times 10^5 \end{aligned} \right\} \text{ By simulation we got these values}$$

$$r_{o5} || r_{o6} = 1.12 \times 10^5$$

$$\begin{aligned} \text{gain 2} &= g_{m5} (r_{o5} || r_{o6}) \\ &\approx (1.63 \times 10^{-4}) (1.12 \times 10^5) \\ &= 18.256 \end{aligned}$$

$$\begin{aligned} \text{net gain} &= (\text{gain 1})(\text{gain 2}) = (104.16)(18.256) \\ &= 1901.54 \end{aligned}$$

$$20 \log(\text{gain}) = 20 \log(1901.54) = 65.58 \text{ dB}$$

let us take $C_2 = 5 \text{ pF}$

$$\begin{aligned} \text{So by the miller effect } (C_2)_{\text{input side}} &= (1+A) C_2 \\ &= (1+18.256)(5 \text{ pF}) \\ &= 96.3 \text{ pF} \end{aligned}$$

$$\begin{aligned} \text{where as } (C_2)_{\text{output side}} &= \frac{C_2}{(1+A)} \\ &= \frac{5 \text{ pF}}{19.256} \\ &= 0.26 \text{ pF} \end{aligned}$$

$$\text{pole 1} \approx \frac{1}{R_{\text{eff}}(C_2)_{\text{input}}} = \frac{1}{2.48 \times 10^5 \times 96.28 \text{ pF}}$$

$$P_1 = 41.8 \text{ kHz}$$

$$\text{pole 2} = \frac{1}{R_{\text{eff}}(C_2)_{\text{output}}} = \frac{1}{1.12 \times 10^5 \times 6 \times 10^{-12}}$$

$$P_2 = 1400 \text{ kHz}$$

	length (μm)	width (μm)
Mref	1	10
M0	1	100
M1	1	21.74
M2	1	21.74
M3	1	2.94
M4	1	2.94
M5	1	5.94
M6	1	100

Mref: $V_{GS} - V_{th} = 0.456 - 0.408 = 0.048$
 $V_{DS} = 0.456$ $V_{DS} > V_{GS} - V_{th}$ $\Rightarrow$ saturation

M0: $V_{GS} - V_{th} = 0.456 - 0.409 = 0.047$
 $V_{DS} = 0.316$ $V_{DS} > V_{GS} - V_{th}$ $\Rightarrow$ saturation

M1: $V_{GS} - V_{th} > V_{DS}$
 $0.584 - 0.5 > 0.5$
 $0.084 > 0.5$ $\Rightarrow$ saturation

M2: $V_{GS} - V_{th} = 0.584 - 0.5 = 0.084$
 $V_{DS} = 0.484$
 $V_{DS} > V_{GS} - V_{th}$ $\Rightarrow$ saturation

$$M3: V_{sg} - V_{tp} < V_{SD}$$

$$0.897 - 0.417 < 0.974$$

$$\boxed{0.557 < 0.974} \Rightarrow \text{Saturation}$$

$$M4: V_{sg} - V_{tp} < V_{SD}$$

$$\boxed{0.897 - 0.417 < 0.974} \rightarrow \text{Saturation}$$

$$M5: V_{sg} - V_{tp} = 1 - 0.418 = 0.582$$


$$\boxed{V_{SD} = 0.904} \Rightarrow \text{Saturation}$$

$$M6: V_{sg} - V_{th} = 0.456 - 0.405 = 0.05$$

$$\boxed{V_{ds} = 0.899V} \Rightarrow \text{Saturation}$$

* all mosfets are in saturation.

* final design of 2stage OTA:-

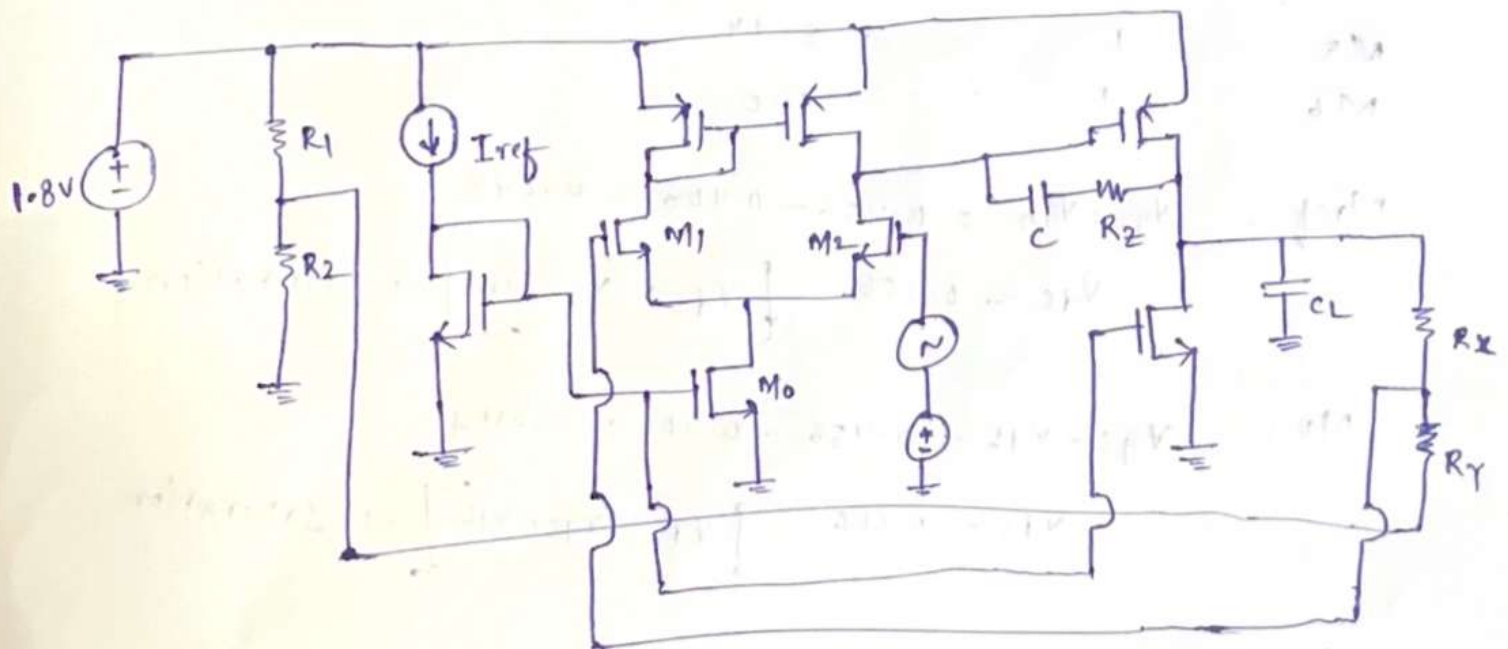

to get 0.9V we can use voltage divider by adding resistors R_1, R_2 . By calculating poles & zeroes C_L taken as $R_x = R_y = 2000 K\Omega \rightarrow$ for closed loop gain

Calculated Bandwidth
(seeing when there is drop at 70%) } Closed loop gain = 2
 } So at 70% = $20 \log(2 \times 0.7)$
 } = 2.94 dB } So gain Bandwidth frequency = 888 kHz

→ Calculated phase margin by checking phase when magnitude is 0dB.

So phase at 0dB :- -104° (approximately) $\Rightarrow \phi_{gc}$

$$\therefore \text{phase margin} = 180^\circ + \phi_{gc} = 76^\circ$$

So my system is stable &

$C_L = 13.55 \text{ pF}$ $C = 50.55 \text{ pF}$ $R_t = 7.5 \text{ k}\Omega$

* for pulse input:-

$$V_{\text{initial}} = 0V$$


$$V_{\text{on}} = 0.2V$$


$$T_{\text{delay}} = 0.1 \text{ msec}$$

$$T_{\text{rise}} = 0.1 \text{ nsec}$$


$$T_{\text{fall}} = 0.1 \text{ msec}$$

∴ The output pulse is:-

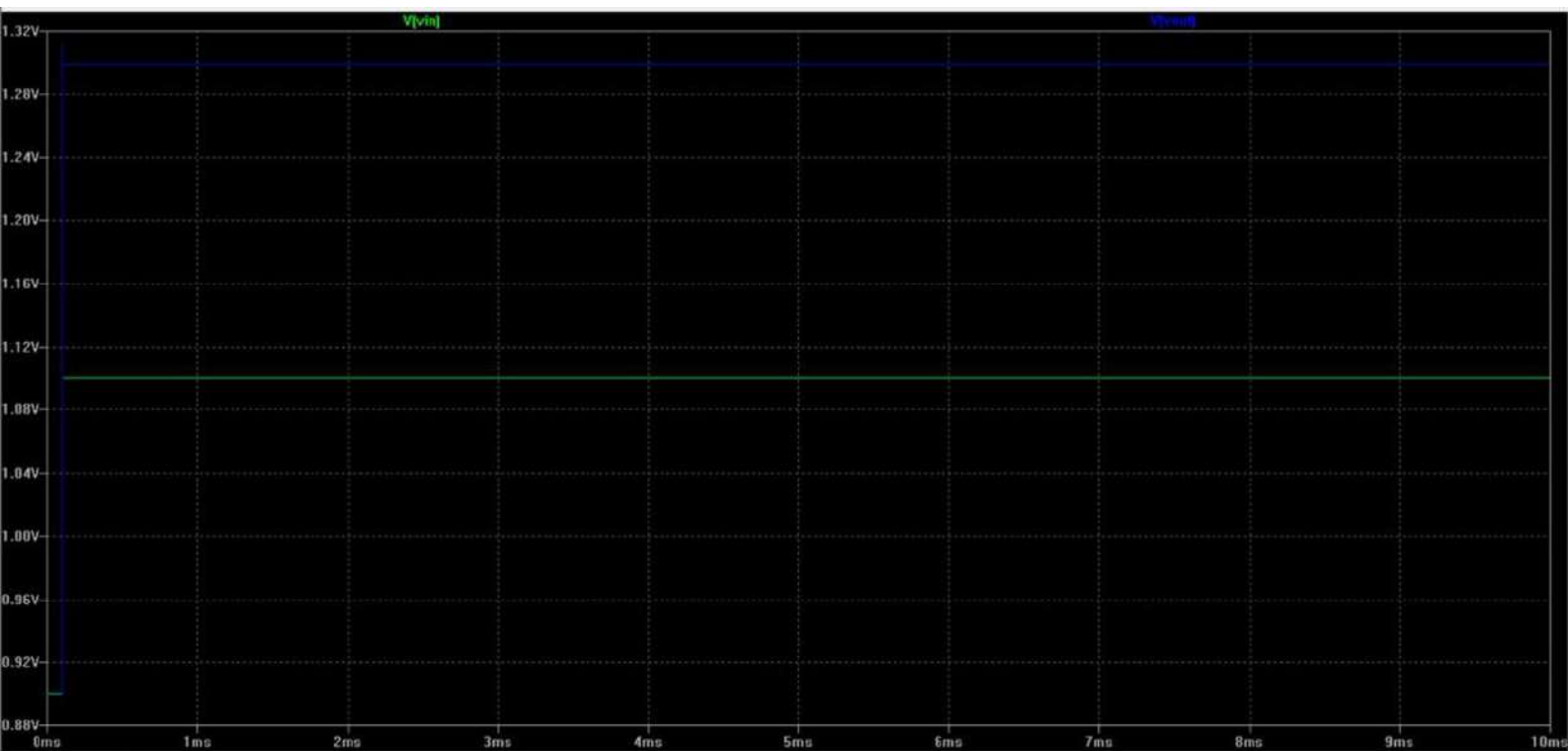

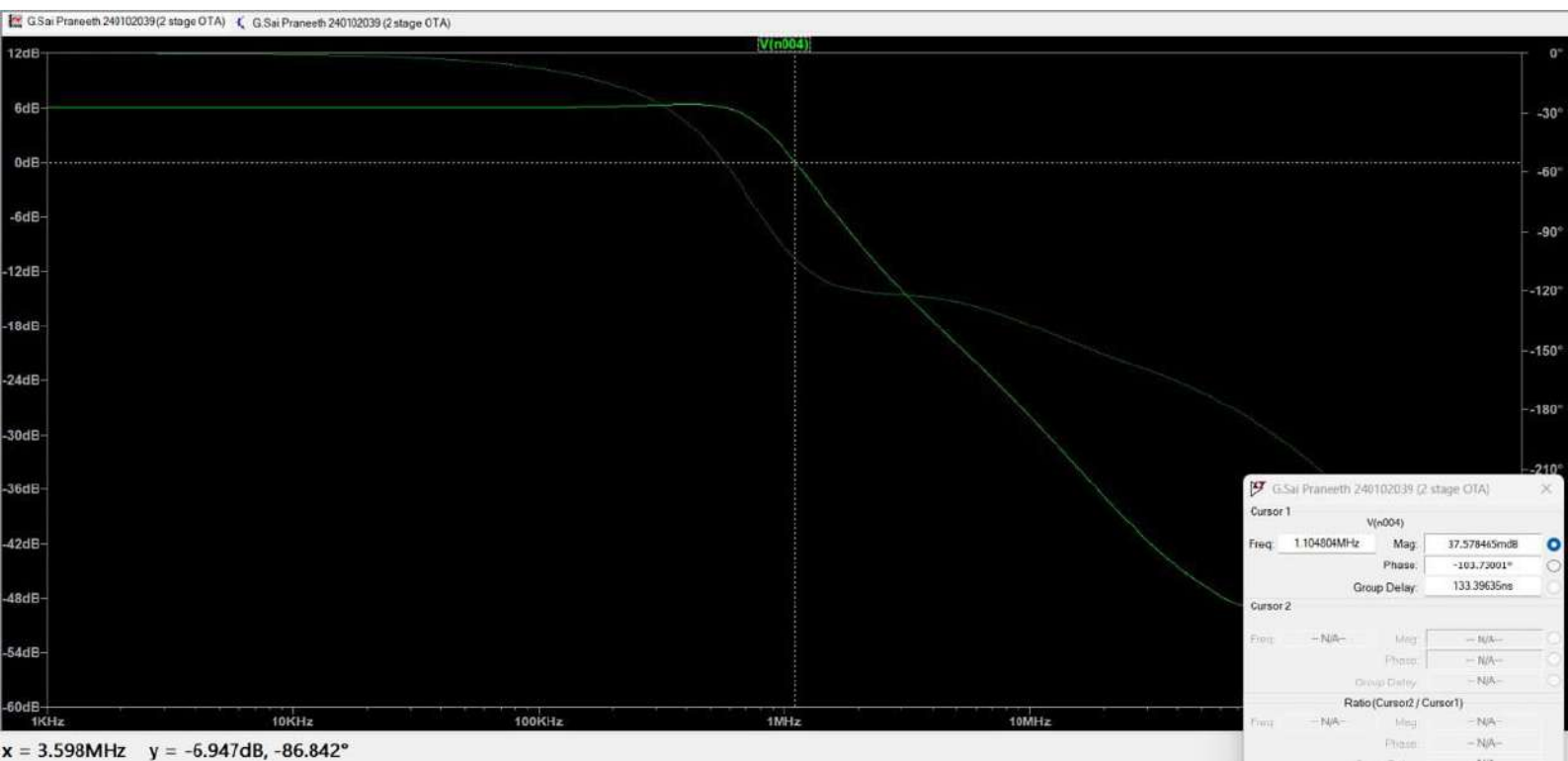

x = 3.598MHz y = -6.947dB, -86.842°

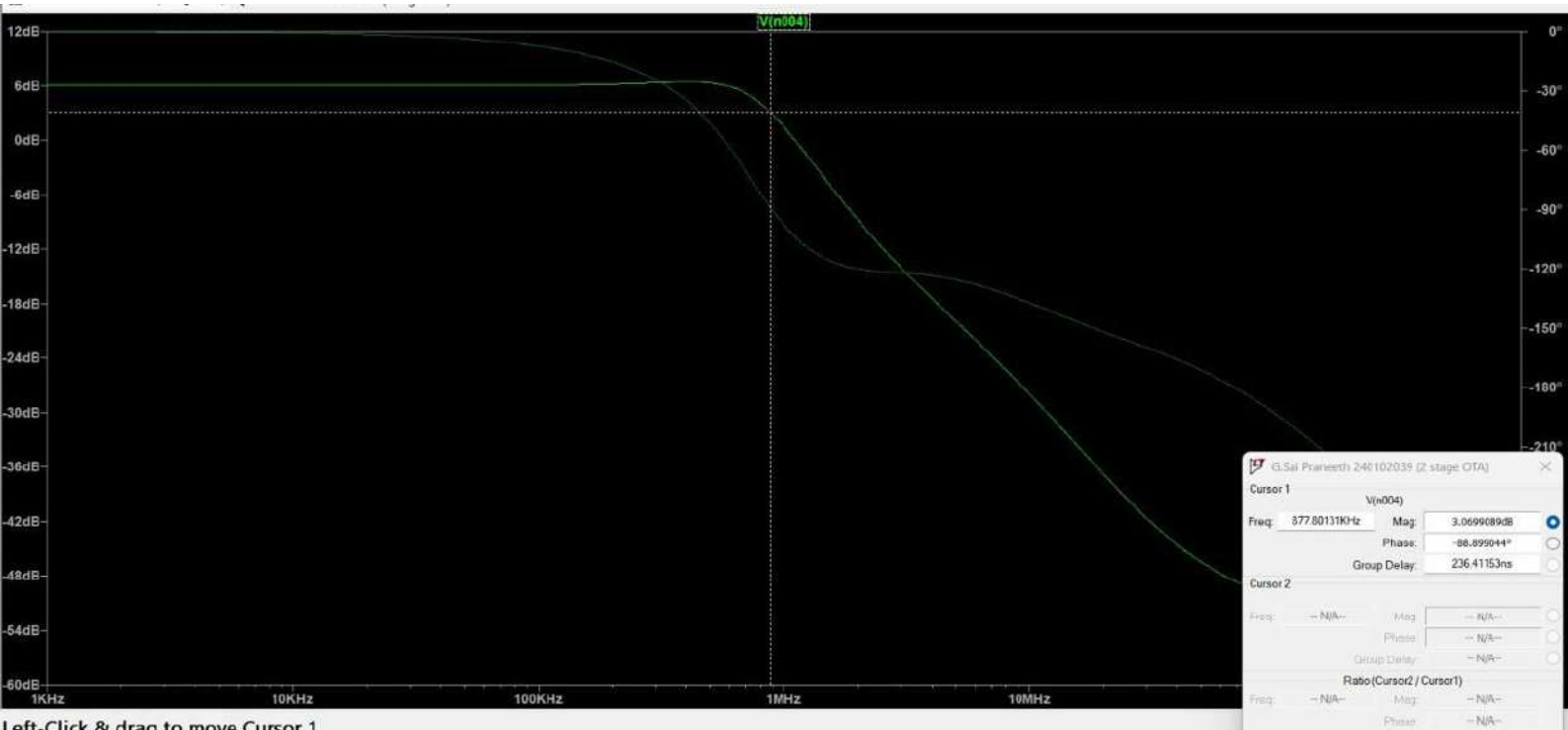

Left-Click & drag to move Cursor 1

